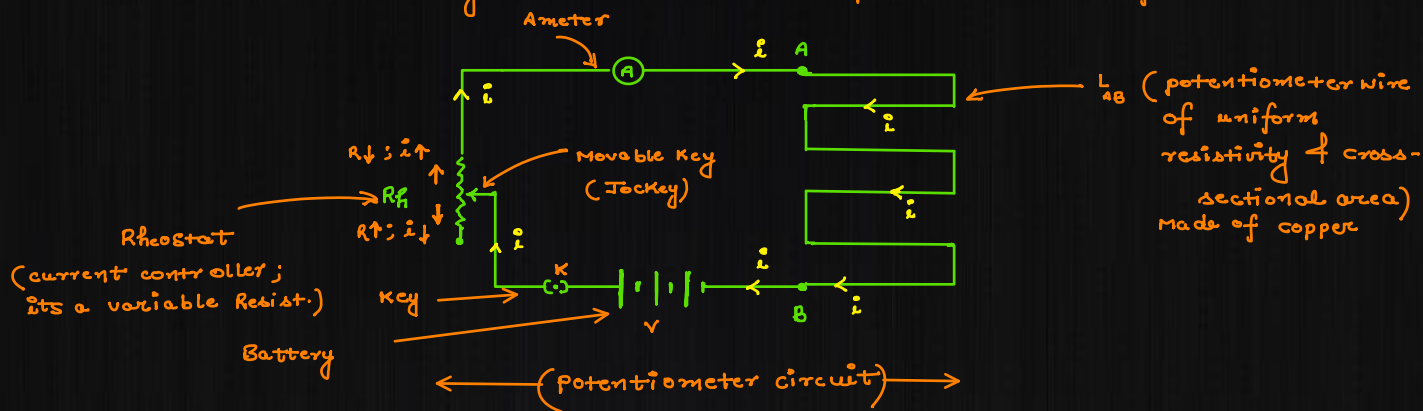


# Potentiometer

05 August 2020 11:30

Potentiometer is a device which is used to determine the EMF & internal resistance of any unknown cell. Using this we can also compare the EMFs of two unknown cells.



P.D. b/w the ends of the potentiometer wire :


$$\begin{aligned}\Delta V_{AB} &= i \times R_{AB} \\ &= i \times \frac{\rho \cdot L_{AB}}{A} \\ \Rightarrow \frac{V_{AB}}{L_{AB}} &= \frac{i \times \rho}{A} = \text{const} \quad (\because \begin{array}{l} i = \text{const} \\ \rho = \text{copper} \\ A = \text{const} \end{array})\end{aligned}$$

i.e. potential gradient or P.D. per unit length of P.M. wire =  $\phi = \left(\frac{i \cdot \rho}{A}\right) = \text{const}$  volt/m

App(I) :  $\rightarrow$  Determination of EMF of any unknown cell :  $\rightarrow$

cell 1 ( $\mathcal{E}_1; r_1$ ) = known

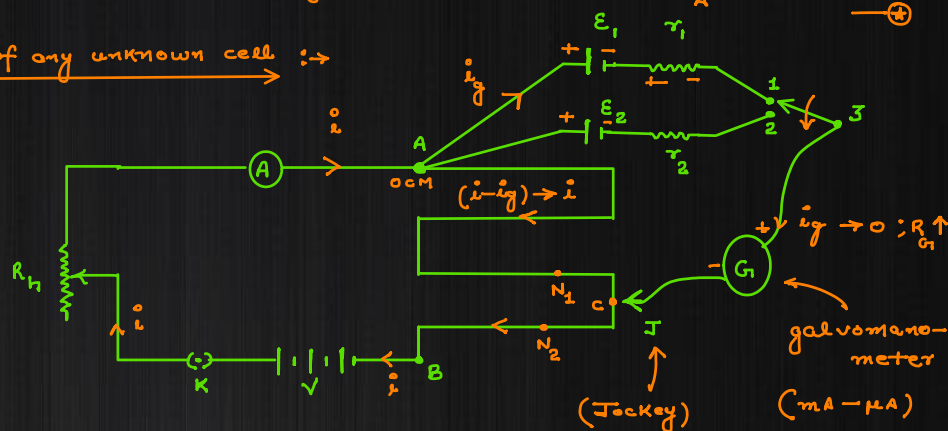cell 2 ( $\mathcal{E}_2; r_2$ ) = unknown



Concept :  $\rightarrow$  we connect any cell with P.M. &  $G$  ; Then we carefully connect the jockey at diff points of the P.M. wire. Due to this the wire's P.D. from A to point of contact becomes equal to the P.D. b/w A to point of contact through cell +  $G$  system.

$$\text{i.e. } (\Delta V_{AC})_{\text{wire}} = (\Delta V_{AC})_{\text{cell} + G}$$

$$\Rightarrow (i - i_g) \times R_{AC} = (\mathcal{E} + i_g \cdot r) + i_g \cdot R_G$$

as we find the null point ;  $i_g = 0$

$$i \times R_{AN} = \mathcal{E} \quad \text{--- (*)}$$

$$\Rightarrow \frac{V_{AB} \times R_{AN}}{R_{AB}} = \mathcal{E}$$

$$\Rightarrow \frac{V_{AB}}{\frac{\rho \times L_{AB}}{A}} \times \frac{l_{AN}}{A} = \mathcal{E}$$

$$\Rightarrow \left(\frac{V_{AB}}{L_{AB}}\right) \times l_{AN} = \mathcal{E}$$

$$\Rightarrow \left\{ \phi \times l_{AN} = \mathcal{E} \right\} ; l_{AN} = \text{length of PM}$$

$$\Rightarrow \left( \frac{V_{AB}}{l_{AB}} \right) \times l_{AN} = \mathcal{E}$$

$$\Rightarrow \boxed{\phi \times l_{AN} = \mathcal{E}}$$

$l_{AN}$  = length of P.M. wire from A to Null point

for the known cell  $\Rightarrow$

$$\mathcal{E}_1 = \phi \times l_{AN_1} \quad \text{--- (1)}$$

$$\text{or} \quad \mathcal{E}_1 = \phi \times l_1$$

ie; Balancing Length.  $l_{AN_1}$  or  $l_1$  is the length of P.M. wire from o.c.m. to the null point

for the unknown cell  $\Rightarrow$

$$\mathcal{E}_2 = \phi \times l_{AN_2}$$

$$\text{or} \quad \mathcal{E}_2 = \phi \times l_2 \quad \text{--- (2)}$$

ie; Balancing length of cell 2 point.  $l_{AN_2}$  or  $l_2$  is the length of P.M. wire from o.c.m. to the null point

eqn (2) / (1)

$$\frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{l_2}{l_1}$$


$$\text{EMF of the unknown cell} \quad \boxed{\mathcal{E}_2 = \mathcal{E}_1 \times \frac{l_2}{l_1}}$$

if  $\mathcal{E}_1$  &  $\mathcal{E}_2$  both are unknown

$$\text{comparison of the EMF} \quad \frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{l_2}{l_1}$$

App (2)  $\Rightarrow$  Determination of internal Resistance of any unknown cell  $\Rightarrow$

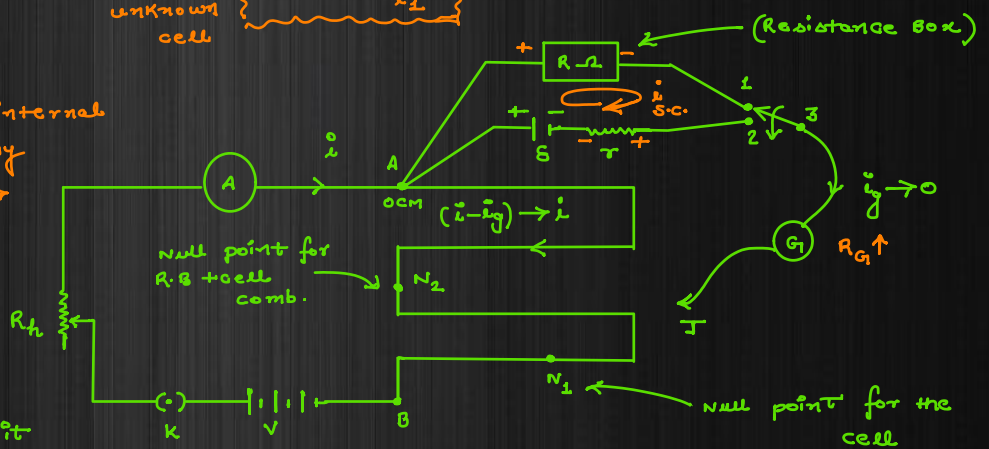first we connect the (G) with the cell only & find the null point for it



$$\Rightarrow \mathcal{E} = \phi \times l_{AN_1}$$

or

$$\Rightarrow \mathcal{E} = \phi \times l_1 \quad \text{--- (1)}$$

$l_{AN_2} = l_2$ ; Balancing length of cell alone

then we connect the R.B. cell & (G) together & find the null point for this combination.

$\therefore$  no current comes out from secondary circuit through the (G) after we found null point.

$\therefore$  we can say no current was gone in the sec. from the primary circuit.

Hence current in the P.M. wire again becomes const. ie;  $i$  Amp. & a short circuit current flows b/w R.B. & the cell

$$i_{sc} = \left( \frac{\mathcal{E}}{R+r} \right) \quad \text{--- (2)}$$

$\therefore$  (G) shows no deflection after we found the null point ie  $i_g \rightarrow 0$

$$\therefore \Delta V_G = i_g \times R_G \rightarrow 0$$

$$\Rightarrow V_{N_2} = V_1 = V_2 = V_3$$

$$\Rightarrow \Delta V_{cell} = \Delta V_{R.B.} = (\Delta V_{wire})_{AN_2}$$

$$\Rightarrow (\mathcal{E} - i_{sc} \times r) = i_{sc} \times R = \phi \times l_{AN_2} \quad \text{--- (3)}$$

from eqn (1)

$l_{AN_2} = l_2$  ie Balancing

$$V_{\text{B.O.}} = \frac{\mathcal{E}}{(R+r)}$$

→ (Cell + R.B.) → SC → AN<sub>2</sub> (1)

from eqn (2)

$$\frac{\mathcal{E} \cdot R}{(R+r)} = \phi \cdot l_2 \quad \text{--- (3)}$$

eqn (3) / (1)

$$\Rightarrow \frac{R}{(R+r)} = \frac{l_2}{l_1}$$

$$\Rightarrow R \cdot l_1 = R \cdot l_2 + r \cdot l_2$$

$$\Rightarrow r \cdot l_2 = R \cdot (l_1 - l_2)$$

internal  
Resistance  
of the  
unknown  
cell.

$$\Rightarrow \boxed{r = R \cdot \left( \frac{l_1}{l_2} - 1 \right)} \quad \text{--- (4)}$$

$l_1 \text{ AN}_2 = l_2$  i.e.  
Balancing  
length of  
(cell + R.B.)

Note: → Here  $l_1 > l_2$ , i.e. Balancing length of the cell alone must be greater than the Balancing length for (cell + R.B.) combination.