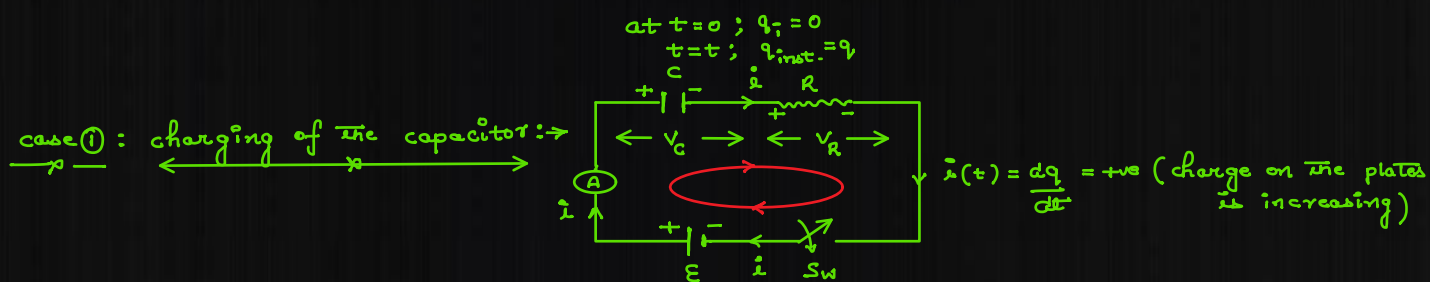


Transient Current

11 August 2020

11:34

"It is the current in a circuit which is a function of time and changes exponentially towards a steady value."



Applying KVL in loop.

$$-\frac{q}{C} - iR + E = 0$$

$$\Rightarrow iR = E - \frac{q}{C}$$

$$\Rightarrow i = \frac{CE - q}{CR}$$

$$\Rightarrow \frac{dq}{dt} = \frac{(CE - q)}{CR}$$

$$\Rightarrow \int_0^q \frac{dq}{(CE - q)} = \int_0^t \frac{dt}{CR}$$

$$\Rightarrow \left[-\log_e \{ CE - q \} \right]_0^q = \left(\frac{t}{CR} \right)_0^t$$

$$\Rightarrow \log_e (CE - q) - \log_e (CE - 0) = -\left(\frac{t-0}{CR} \right)$$

$$\Rightarrow \log_e \left\{ \frac{CE - q}{CE} \right\} = -\frac{t}{CR}$$

$$\Rightarrow \frac{CE - q}{CE} = e^{-t/CR}$$

$$\Rightarrow CE - q = CE \cdot e^{-t/CR}$$

$$\text{instantaneous charge on the plates of the capacitor} \Rightarrow q = CE \cdot (1 - e^{-t/CR}) \quad \text{--- (*)}$$

Let $CE = q_0$ or q_{max} ; max. charge on the plates

Let $CR = \tau$; time constant (unit $\rightarrow \text{sec}$; $\text{SF} \rightarrow [T]$)

\therefore inst. charge on the plates

$$q = q_0 (1 - e^{-t/\tau}) \quad \text{--- (*)}$$

$$\text{as } i = \frac{dq}{dt} = q_0 \cdot \left\{ 0 - \left(e^{-t/\tau} \right) \times -\frac{1}{\tau} \right\}$$

$$\Rightarrow i = \frac{q_0}{\tau} \cdot e^{-t/\tau}$$

$$= \frac{CE}{CR} \cdot e^{-t/\tau}$$

$$\Rightarrow i = \frac{E}{R} \cdot e^{-t/\tau}$$

$$\text{here } \frac{E}{R} = i_0 \text{ or } i_{max}$$

$$\text{inst. current (ie; transient)} \Rightarrow i = i_0 \cdot e^{-t/\tau} \quad \text{--- (*)}$$

inst. current $\Rightarrow i = i_0 \cdot e^{-t/\tau}$ — (*)
(ie; transient current)

instantaneous p.d. across the capacitor (v_c) = $\frac{q_0}{C} = \frac{C\varepsilon}{C} \cdot (1 - e^{-t/\tau})$
 $\Rightarrow v_c = \varepsilon \cdot (1 - e^{-t/\tau})$ — (*)

instantaneous p.d. across the resistance (v_R) = $i \times R = \frac{\varepsilon \times e^{-t/\tau}}{R} \times R$
 $\Rightarrow v_R = \varepsilon \cdot e^{-t/\tau}$ — (*)

imp points \Rightarrow i) at $t=0$; initially as the switch is closed.

* charge on the plates (q) = $q_0 \cdot (1 - e^0)$
 $= q_0 \cdot (1 - 1)$
 $\Rightarrow q_0 = 0$

* current in the circuit (i) = $i_0 \cdot e^0$
 $\Rightarrow i = i_0 = \frac{\varepsilon}{R} = \text{max}$

* p.d. b/w the plates of the capacitor (v_c) = $\varepsilon \cdot (1 - e^0)$
 $= \varepsilon \cdot (1 - 1)$
 $\Rightarrow v_c = 0$

* p.d. b/w the plates of the resistor (v_R) = $\varepsilon \cdot e^0$
 $\Rightarrow v_R = \varepsilon$

"at $t=0$, the capacitor act like 'short-circuit' & the current in the circuit becomes maximum."

ii) at $t \rightarrow \infty$; after a long time after the switch (ie steady state) \Rightarrow

* charge on the plates of the capacitor
 $q = q_0 \cdot (1 - e^{-\infty})$
 $= q_0 \cdot (1 - \frac{1}{e^{\infty}})$
 $= q_0 \cdot (1 - \frac{1}{\infty})$
 $= q_0 \cdot (1 - \frac{1}{0})$
 $\therefore q = q_0 \text{ or } C\varepsilon$

* current in the circuit (i) = $i_0 \cdot e^{-\infty}$
 $= \frac{i_0}{\infty}$
 $\therefore i = 0$


* p.d. b/w the plates of the capacitor (v_c) = $\varepsilon \cdot (1 - e^{-\infty})$
 $= \varepsilon \cdot (1 - \frac{1}{\infty})$
 $= \varepsilon \cdot (1 - 0)$
 $\therefore v_c = \varepsilon$

* p.d. b/w the ends of the resistor (v_R) = $\varepsilon \cdot e^{-\infty}$
 $= \frac{\varepsilon}{\infty}$
 $\therefore v_R = 0$

"at steady state ie: $t \rightarrow \infty$, the capacitor becomes open circuit"

∴ at steady state i.e. $t \rightarrow \infty$, the capacitor becomes open circuit hence the capacitor acts as open circuit.

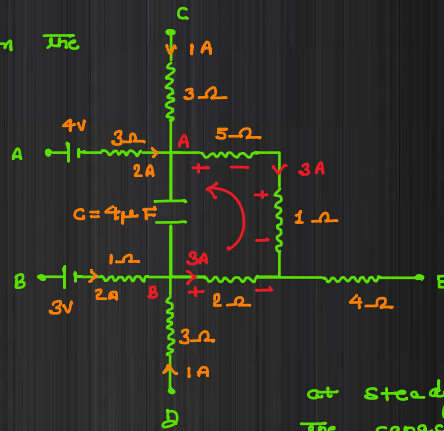Q: find the energy stored in the capacitor.



at steady state;
the capacitor is open circuit

P.D. b/w points A & B after removing the capacitor

$$\Delta V_{AB} = (-3 \times 2) + (3 \times 1) + (3 \times 5)$$

$$= -6 + 3 + 15$$

$$\Rightarrow \Delta V_{AB} = 12 \text{ volt} \quad \text{--- (1)}$$

∴ Energy stored in the capacitor

$$U = \frac{1}{2} \cdot C \cdot \Delta V_{AB}^2$$


$$= \frac{1}{2} \times 4 \times 10^{-6} \times (12)^2$$

$$= 2 \times 10^{-6} \times 144$$


$$\therefore U = 288 \mu\text{J}$$

Q: → find the current shown by the (A) at i) $t = 0\text{s}$; i.e. just after closing the switch
ii) $t \rightarrow \infty$; i.e. at steady state.


Sol: →

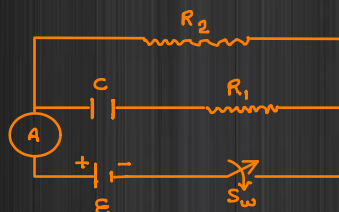

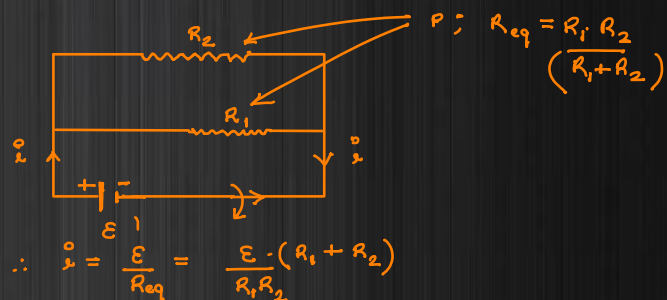i) at $t = 0$; capacitor is short circuit:




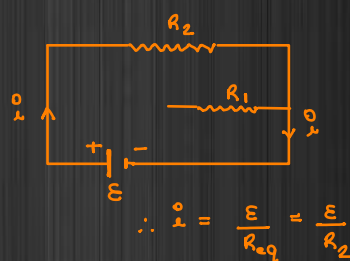ii) at $t \rightarrow \infty$, capacitor becomes open circuit.



Q: find the Time constant of the above circuit.

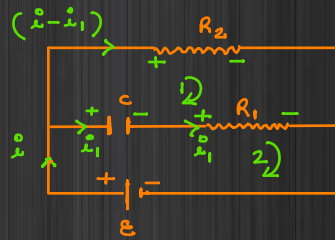Q: find the time constant of the above circuit.



KVL in loop 1: $\rightarrow - (i - i_1) \cdot R_2 + i_1 \cdot R_1 + \frac{q}{C} = 0$

$$i_1 \cdot R_1 = (i - i_1) \cdot R_2 + \frac{q}{C} \quad \text{--- (1)}$$

KVL in loop 2: $\rightarrow -\frac{q}{C} - i_1 \cdot R_1 + \varepsilon = 0$

$$\Rightarrow i_1 \cdot R_1 = \varepsilon - \frac{q}{C}$$

$$\Rightarrow i_1 = \left(\frac{C\varepsilon - q}{C R_1} \right)$$

$$\frac{dq}{dt} = \left(\frac{C\varepsilon - q}{C R_1} \right)$$

$$\Rightarrow \int_0^q \left(\frac{dq}{C\varepsilon - q} \right) = \int_0^t \frac{dt}{C R_1}$$

$$\Rightarrow - \left\{ \log_{de} (C\varepsilon - q) \right\}_0^q = \left(\frac{t}{C R_1} \right)_0^t$$


$$\Rightarrow \log_{de} \left(\frac{C\varepsilon - q}{C\varepsilon} \right) = - \left(\frac{t - 0}{C R_1} \right)$$

$$\Rightarrow \frac{C\varepsilon - q}{C\varepsilon} = e^{-t/C R_1}$$


$$\Rightarrow q = C\varepsilon \cdot (1 - e^{-t/C R_1})$$

$$\therefore \tau = C R_1$$

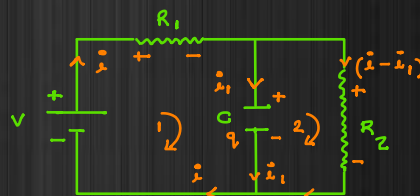
Q: the switch shown in the following fig. is closed at $t=0$; if the instantaneous charge on the plates is $q = q_0 \cdot (1 - e^{-\alpha t})$. find q_0 & α .
also find the current drawn from the battery at $t=0$ & $t \rightarrow \infty$




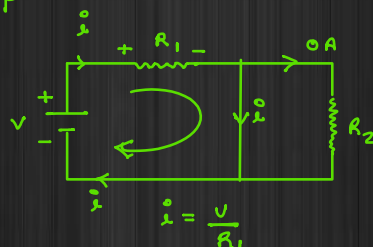Solⁿ: \Rightarrow at $t=0$; capacitor is short circuited; $(i - i_1)$



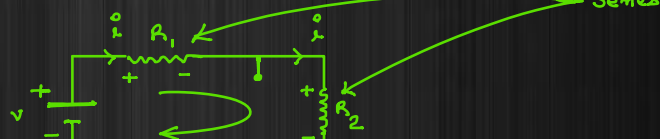at $t \rightarrow \infty$; capacitor is open circuited



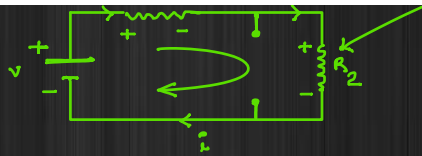

$$\therefore i = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{(R_1 + R_2)}$$

let the instantaneous charge on the plates of the capacitor is 'q'.

KVL in loop 1 \rightarrow

$$-i \cdot R_1 - \frac{q}{C} + V = 0$$

$$\Rightarrow i = \left(\frac{CV - q}{CR_1} \right) \quad \text{--- (1)}$$

KVL in loop 2 \rightarrow

$$-(i - i_1) \cdot R_2 + \frac{q}{C} = 0$$

$$\Rightarrow -i R_2 + i_1 R_2 + \frac{q}{C} = 0$$

from (1);

$$\Rightarrow -R_2 \cdot \left(\frac{CV - q}{CR_1} \right) + i_1 R_2 + \frac{q}{C} = 0$$

$$\Rightarrow q \cdot \left\{ \frac{R_2}{CR_1} + \frac{1}{C} \right\} - \frac{CV R_2}{CR_1} + i_1 R_2 = 0$$

$$\Rightarrow i_1 R_2 = \frac{V R_2}{R_1} - q \cdot \left\{ \frac{R_2 + R_1}{CR_1} \right\}$$

$$\Rightarrow i_1 = \frac{CV R_2 - q(R_2 + R_1)}{CR_1 R_2}$$

$$\therefore i_1 = \frac{dq}{dt}$$

$$\Rightarrow \frac{dq}{dt} = \frac{CV R_2 - q(R_1 + R_2)}{CR_1 R_2}$$

$$\Rightarrow \int_0^q \frac{dq}{CV R_2 - q(R_1 + R_2)} = \int_0^t \frac{dt}{CR_1 R_2}$$

$$\Rightarrow \left[-\log_e \left\{ \frac{CV R_2 - q(R_1 + R_2)}{CV R_2} \right\} \right]_0^q = \frac{1}{CR_1 R_2} \cdot (t)_0^t$$

$$\Rightarrow \log_e \left\{ \frac{CV R_2 - q(R_1 + R_2)}{CV R_2} \right\} - \log_e \frac{CV R_2}{CV R_2} = \frac{-t}{CR_1 R_2} (R_1 + R_2)$$

$$\Rightarrow \log_e \left\{ \frac{CV R_2 - q(R_1 + R_2)}{CV R_2} \right\} = \frac{-t \cdot (R_1 + R_2)}{CR_1 R_2}$$

$$\Rightarrow \frac{CV R_2 - q(R_1 + R_2)}{CV R_2} = e^{\frac{-t}{CR_1 R_2}}$$

$$\Rightarrow q(R_1 + R_2) = CV R_2 \cdot \left\{ 1 - e^{\frac{-t}{CR_1 R_2}} \right\}$$

$$\therefore q = \frac{CV R_2}{(R_1 + R_2)} \cdot \left\{ 1 - e^{\frac{-t}{CR_1 R_2}} \right\}$$

comparing with; $q = q_0 \cdot (1 - e^{-\alpha t})$

$$q_0 = \frac{CV R_2}{(R_1 + R_2)} ; \alpha = \frac{(R_1 + R_2)}{CR_1 R_2} \text{ or } \frac{1}{\tau}$$

iii) at $t = \tau$ or CR :

*) charge on the plates of the capacitor;

$$q = q_0 \cdot (1 - e^{-\tau/\tau})$$

$$\begin{aligned}
 q &= q_0 \cdot (1 - e^{-t/\tau}) \\
 &= q_0 \cdot (1 - e^{-1}) \\
 &= q_0 \left(1 - \frac{1}{e}\right) \quad \because e = 2.71 \\
 &= 0.63 q_0
 \end{aligned}$$


$$\Rightarrow q = 63\% \text{ of } q_0$$

$$\begin{aligned}
 \star) \text{ current in the circuit ; } i &= i_0 \cdot e^{-t/\tau} \\
 &= i_0 \cdot e^{-1} \\
 &= \frac{i_0}{e} \\
 &= 0.37 \cdot i_0 \\
 \Rightarrow i &= 37\% \text{ of } i_0
 \end{aligned}$$


$$\begin{aligned}
 \star) \text{ P.D. b/w the plates of the capacitor ; } \\
 v_c &= \varepsilon \cdot (1 - e^{-t/\tau}) \\
 &= \varepsilon \left(1 - \frac{1}{e}\right) \\
 &= 0.63 \varepsilon \\
 \therefore v_c &= 63\% \text{ of } \varepsilon
 \end{aligned}$$

$$\begin{aligned}
 \star) \text{ P.D. across the resistor ; } \\
 v_R &= \varepsilon \cdot e^{-t/\tau} \\
 &= \varepsilon \cdot e^{-1} \\
 &= \frac{\varepsilon}{e} \\
 &= 0.37 \cdot \varepsilon \\
 \therefore v_R &= 37\% \text{ of } \varepsilon
 \end{aligned}$$

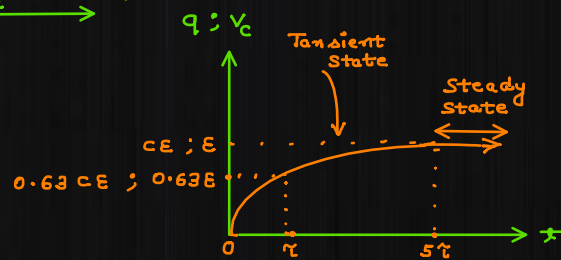iv) \longleftrightarrow Graph of q & v_c vs t : \rightarrow



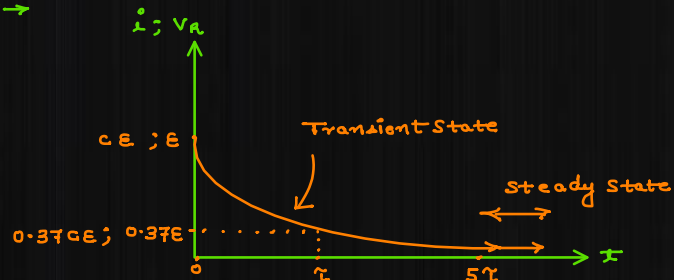\longleftrightarrow Graph of i & v_R vs t : \rightarrow



Steady state achieves at $t > 5\tau$