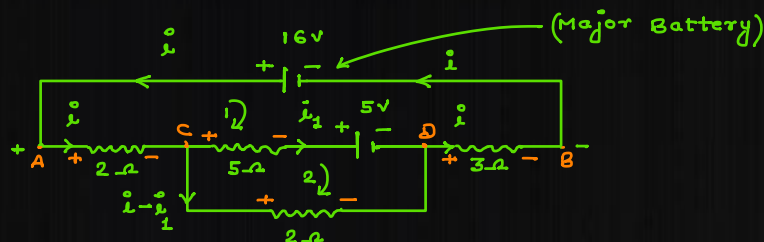


Electric Current

02 August 2020 11:30

Q: → Find the electric current through the 5 volt cell.



$$\begin{aligned} \text{KVL in loop ①:} \rightarrow \\ -16 + 3i + 5 + 5i_1 + 2i = 0 \\ \Rightarrow 5i + 5i_1 = 11 \text{ --- ①} \end{aligned}$$


$$\begin{aligned} \text{KVL in loop ②:} \rightarrow \\ -5i_1 - 5 + 2(i - i_1) = 0 \\ \Rightarrow 2i - 7i_1 = 5 \text{ --- ②} \end{aligned}$$

$$\begin{aligned} \text{eqn ①} \times 2 - \text{eqn ②} \times 5 \\ \hline 10i + 10i_1 = 22 \\ -10i - 35i_1 = -25 \\ \hline 45i_1 = -3 \end{aligned}$$

$$\therefore i_1 = -\frac{1}{15} \text{ A} \quad \left(\frac{1}{15} \text{ A from D to C} \right)$$

Q: → In the given circuit, the power developed across the 5Ω resistor is 45 Watts. Find.

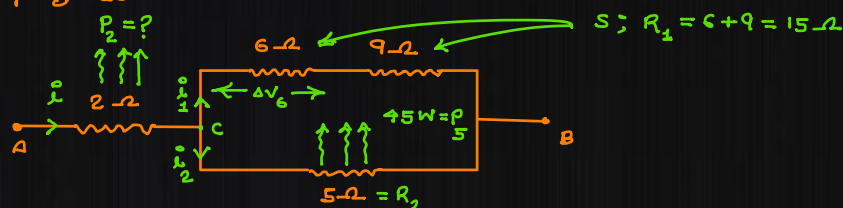- Power developed in 2Ω resistance.
- P.D. across the 6Ω resistance.



$$\begin{aligned} \text{at junc. C:} \rightarrow \\ \frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{5}{15} = \frac{1}{3} \text{ --- ①} \end{aligned}$$

$$\therefore \text{power developed across } 5\Omega \text{ (P}_5\text{)} = i_2^2 \cdot R = 45$$

$$\Rightarrow i_2^2 \times 5 = 45$$

$$\Rightarrow i_2^2 = 9$$

$$\therefore i_2 = 3 \text{ Amp. --- ②}$$

$$\text{from ① \& ②:} \rightarrow$$

$$i_1 = 1 \text{ A}$$

$$\therefore i = i_1 + i_2 = 4 \text{ A}$$

$$\therefore \text{power developed across } 2\Omega$$

$$P_2 = i^2 \times R = 16 \times 2 = 32 \text{ watt}$$


$$\& \text{ P.D. across } 6\Omega \text{ (}\Delta V_6\text{)} = i_1 \times R = 1 \times 6 = 6 \text{ volt.}$$


Q: find the equivalent capacitance b/w points A & B.

i)




1, 2, 3 are in parallel combination

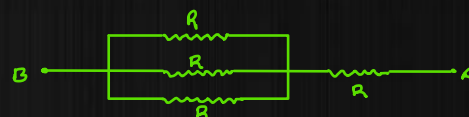

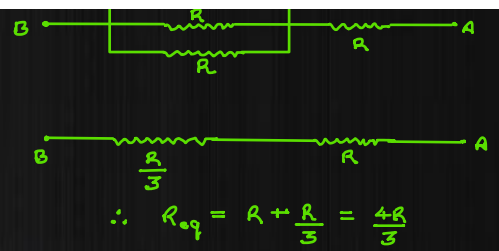

ii)


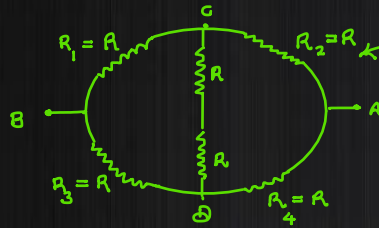


Balanced wheat-stone bridge

$$\therefore \frac{R_1}{R_2} = \frac{R_3}{R_4}$$


$$\therefore V_C = V_D \Rightarrow \Delta V_{CD} = 0$$

hence Branch CD can be open circuit.

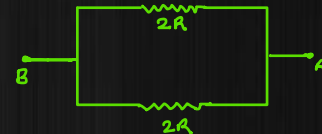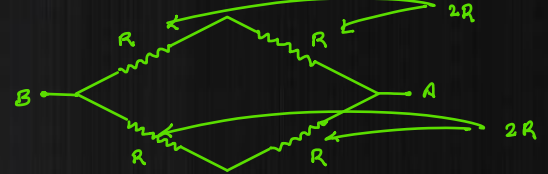


$$\therefore R_{eq} = \frac{2R}{2} = R$$

iii)

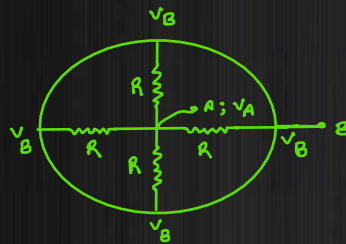


\Rightarrow

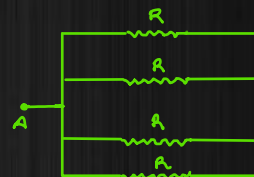




$$\therefore R_{eq} = \frac{R}{4}$$

Q: find the resistance b/w points A & B. Each branch of the cube is of $R \Omega$.


i)

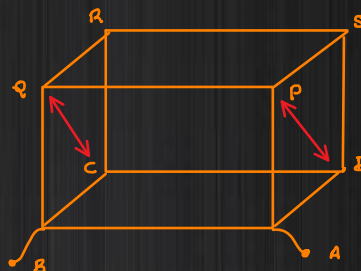

here: $V_Q = V_C \neq V_P = V_D$

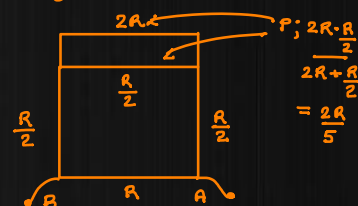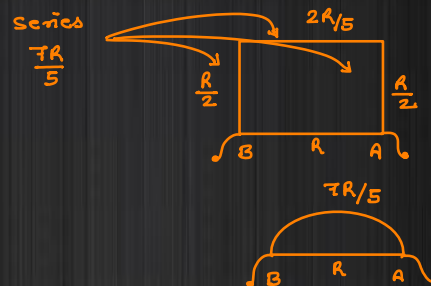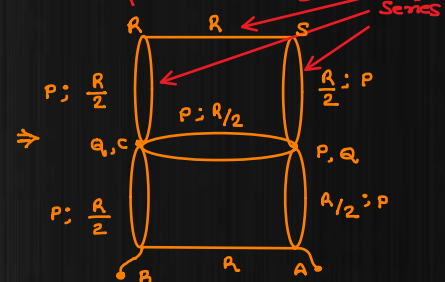

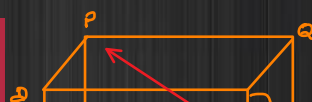
$$\therefore R_{eq} = \frac{\frac{7R}{5} \cdot R}{\frac{7R}{5} + R} = \frac{7R}{12} \Omega$$






here: $V_P = V_R \neq V_D = V_C$

ii)

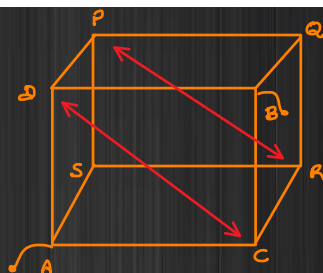


here: $V_P = V_R$ & $V_D = V_C$

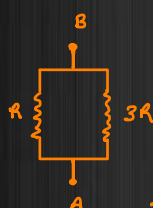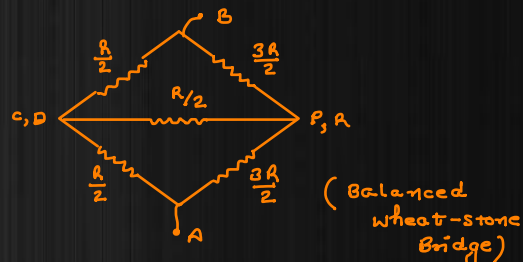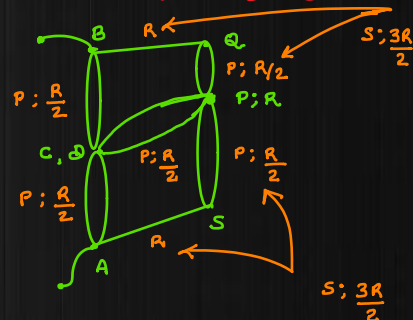

$$\therefore R_{eq} = \frac{R \times 3R}{R + 3R} = \frac{3R}{4}$$

Q: What will be change in resistance of the circuit consisting 5 resistances, if 2 identical resistances are added as shown by the dashed lines?

Solⁿ! →

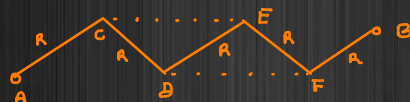


Let resistance of each segment is R
as all segments are in series
 $\therefore R_{eq} = 5R$ — ①


after joining
C-E & D-F



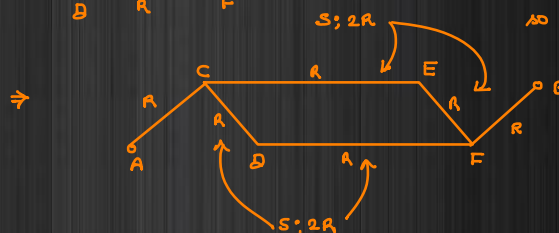The circuit b/w C & F is a balanced
Wheatstone bridge
so we can remove DE



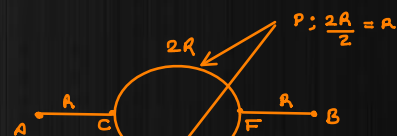
$$\therefore \frac{R_{eq}'}{R_{eq}} = \frac{3}{5}$$




$$\therefore R_{eq}' = 3R$$
 — ②

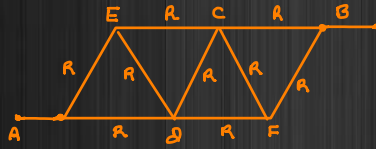Q: Determine the resistance b/w A & B. Resistance of each segment is R.



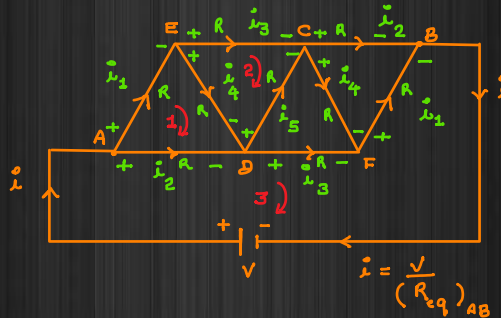Solⁿ: \rightarrow considering an imaginary battery across A & B.



its a problem based upon reverse symmetry.

KVL in loop 1: \rightarrow

$$-i_1 \cdot R - i_4 \cdot R + i_2 \cdot R = 0$$

$$\Rightarrow i_2 = i_1 + i_4 \quad \text{--- (1)}$$

KVL in loop 2: \rightarrow

$$-i_3 \cdot R + i_5 \cdot R + i_4 \cdot R = 0$$

$$\Rightarrow i_3 = i_4 + i_5 \quad \text{--- (2)}$$

at j'n. D from KCL: \rightarrow

$$i_2 + i_4 = i_3 + i_5 \quad \text{--- (3)}$$

from (2) & (3)

$$i_2 + i_4 = i_4 + i_5 + i_5$$

$$\Rightarrow i_2 = 2i_5 \quad \text{--- (4)}$$

$$\text{at j'n. E; } i_1 = i_3 + i_4 \quad \text{--- (5)}$$

from (2) & (1)

$$i_2 - i_4 = i_4 + i_5 + i_4$$

from (4)

$$2i_5 = 3i_4 + i_5$$

$$\Rightarrow i_4 = \frac{i_5}{3}$$

from (3)

$$2i_5 + \frac{i_5}{3} = i_3 + i_5$$

$$\therefore i_3 = \frac{i_5}{3} + \frac{i_5}{3}$$

$$\Rightarrow i_3 = \frac{2i_5}{3}$$

$$\text{from (5); } i_1 = \frac{2i_5}{3} + \frac{i_5}{3}$$


$$\therefore i_1 = \frac{3i_5}{3}$$

$$\text{at j'n. A: } i = i_1 + i_2$$

$$\text{at pt A: } i = i_1 + i_2 \\ = \frac{5i_5}{3} + 2i_5 \\ \Rightarrow i = \frac{11i_5}{3} \quad \text{--- (6)}$$


$$\text{KVL in loop (3)} \Rightarrow -i_2 R - i_3 R - i_1 R + V = 0 \\ V = R \cdot (i_1 + i_2 + i_3) \\ \Rightarrow i R_{eq} = R \cdot \left(\frac{5i_5}{3} + 2i_5 + \frac{4i_5}{3} \right) \\ \Rightarrow \frac{11i_5}{3} R = \frac{R}{2} \times (15i_5) \\ \Rightarrow R_{eq} = \frac{15}{11} R \quad \underline{\text{Ans.}}$$

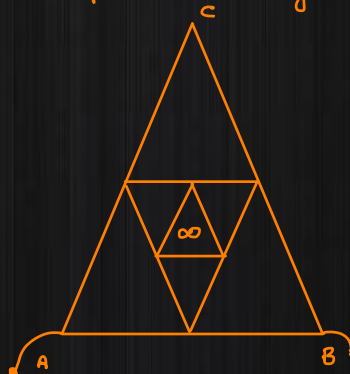Q: find the equivalent resistance b/w points A & B, assuming that the successive embedded equilateral triangles (with side length decreasing by half), tends to infinity. Side length of the outer triangle is 'a' & resistance per unit length is 'r' a.m!





here ; $R_{AB} = R_{BC} = R_{CA} = a \cdot r = R$ (let) --- (1)

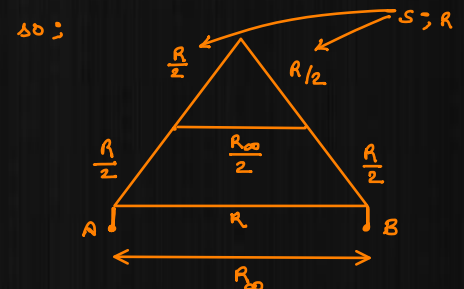
It's an infinite series where each next inner triangle is of half resistance of the preceding Δ .


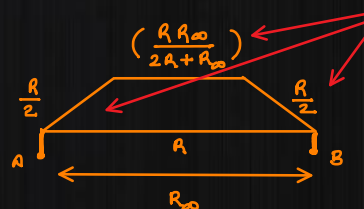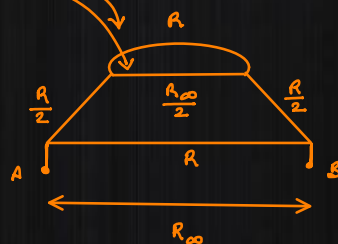
$$\frac{R \cdot \frac{R_00}{2}}{R + \frac{R_00}{2}} = \frac{R \cdot R_00}{2R + R_00} ; P$$


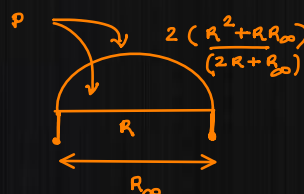
$$S ; \frac{\frac{R}{2} + \frac{R}{2} + \frac{R \cdot R_00}{2R + R_00}}{2R + R_00} \\ = \frac{2R^2 + R R_00 + R R_00}{(2R + R_00)} \\ = \frac{2(R^2 + R R_00)}{(2R + R_00)}$$



$$\therefore \frac{1}{R_00} = \frac{1}{R} + \frac{(2R + R_00)}{2(R^2 + R R_00)} \\ \frac{1}{R_00} = \frac{(2R^2 + 2R R_00 + 2R^2 + R R_00)}{2R \cdot (R^2 + R R_00)} \\ \frac{1}{R_00} = \frac{4R^2 + 3R R_00}{2R(R^2 + R R_00)}$$

$$\Rightarrow 2R^3 + 2R^2 R_\infty = 4R^2 R_\infty + 3R R_\infty^2$$

$$\Rightarrow 3R_\infty^2 + 2R R_\infty - 2R^2 = 0$$

$$\Rightarrow R_\infty = \frac{-2R \pm \sqrt{4R^2 + 24R^2}}{6}$$

$$\Rightarrow R_\infty = \frac{R}{6} (2\sqrt{7} - 2) = \frac{R(\sqrt{7} - 1)}{3}$$

$$\therefore R_\infty = \frac{(\sqrt{7} - 1)}{3} \cdot a \cdot r \quad -2$$

H.W. Solve The Marked Problems \rightarrow