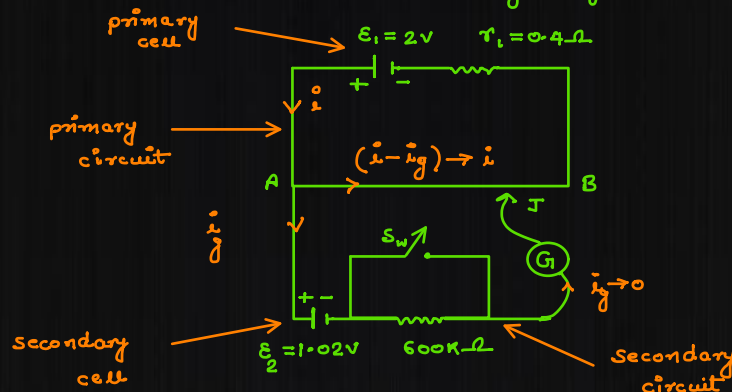


# Potentiometer

07 August 2020 11:32

Q: The figure shows a potentiometer with a cell of EMF 2V & internal resistance  $0.4\Omega$  maintaining a constant potential difference across the potentiometer wire AB. A standard (i.e. ideal) cell of EMF 1.02V gives a balance point at 67.3 cm length of the wire. To ensure very low current drawn from the standard cell a very high resistance of  $600k\Omega$  is put in the series with it, which is short-circuited very close to the balancing point, then the cell is replaced with another cell of EMF  $\epsilon$  volts & the null point is found at 82.3 cm. Find:

- EMF  $\epsilon$  of the cell
- why the  $600k\Omega$  resistance is connected in series
- what will the new balancing length be if the switch is closed.



The  $600k\Omega$  resistance is used to make sure no current pass through the secondary circuit i.e.  $i_g \rightarrow 0$ , so the potential gradient of the P.M. wire remain same as before connecting the Jockey on the wire.

for cell 1

$$\epsilon_1 = \phi \cdot l_1 \quad \text{--- (1)}$$

for cell 2

$$\epsilon_2 = \phi \cdot l_2 \quad \text{--- (2)}$$

from (2) / (1)

$$\frac{\epsilon_2}{\epsilon_1} = \frac{l_2}{l_1}$$

$$\epsilon_2 = \epsilon_1 \times \frac{l_2}{l_1}$$

$$= 1.02 \times \frac{82.3}{67.3}$$

$$\text{EMF of the unknown cell} \Rightarrow \epsilon_2 = 1.25 \text{ volt}$$

Potential gradient of the wire

$$\phi = \frac{V}{L} = \frac{\epsilon}{l_1} = \frac{1.02}{0.673} = 1.52 \frac{V}{m} \quad \text{--- (3)}$$

if we close the switch,  $600k\Omega$  becomes short circuited as we found the new null points

$$\epsilon_1 = \phi \cdot l'_1 \quad \& \quad \epsilon_2 = \phi \cdot l'_2$$

$\therefore \phi = \text{const}$  & do not change

$$\text{so } l'_1 = \frac{\epsilon_1}{\phi} = \frac{1.02}{1.52} = 0.67m \quad \& \quad l'_2 = \frac{\epsilon_2}{\phi} = \frac{1.25}{1.52} = 0.82m$$

ie; Balancing length of both the cells will remain same.

Q:  $\rightarrow$  In the following P.M. circuit comparison of 2 resistances is done. Balance point of the standard resistor  $R = 10\Omega$  is at 58.3 cm, while the balance point of the unknown resistance  $X$  is found at 68.5 cm. Find the value of  $X$  if the null point of the cell is found at 78.4 cm.

of the standard resistor  $R = 10\ \Omega$  is at  $58.3\text{ cm}$ , while the balance point of the unknown resistance  $x$  is found at  $68.5\text{ cm}$ . Find the value of  $x$  if the null point of the cell is found at  $78.4\text{ cm}$ .

Sol<sup>n</sup>  $\Rightarrow$  Given;  $l_{\text{cell}} = 78.4\text{ cm}$

When we connect  $R$  with cell & balance;


$$r = R \cdot \left\{ \frac{l_c}{l_{c+R.B}} - 1 \right\}$$

$$= 10 \times \left\{ \frac{78.4}{58.3} - 1 \right\}$$

$$r = 10 \times 0.34$$

$$\therefore r = 3.4\ \Omega \quad \text{--- (1)}$$

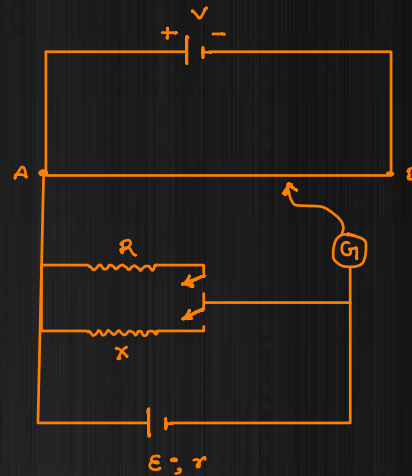Internal resistance of the secondary cell



When we balance  $x$  with the cell;

$$r = x \cdot \left\{ \frac{l_c}{l_{c+R.B}} - 1 \right\}$$

$$3.4 = x \cdot \left\{ \frac{78.4}{68.5} - 1 \right\}$$

$$3.4 = x \cdot 0.14$$

$$\therefore x = \frac{3.4}{0.14} = 24.3\ \Omega$$

Q: In the following P.M. circuit, open circuit balance point of the cell is found at  $76.3\text{ cm}$ , when a resistor of  $9.5\text{ K}\Omega$  is used in parallel with the cell the balance point shifts to  $64.8\text{ cm}$ . Find the internal resistance of the cell.

$$\therefore \frac{l}{l_{\text{cell}}} = 76.3\text{ cm}$$

$$\frac{l}{l_{c+R.B}} = 64.8\text{ cm}$$

$$R = 9.5\text{ K}\Omega$$


$$\therefore r = R \cdot \left\{ \frac{l_c}{l_{c+R.B}} - 1 \right\}$$

$$= 9.5 \times 10^3 \times \left\{ \frac{76.3}{64.8} - 1 \right\}$$


$$= 9.5 \times 10^3 \times 0.18$$

$$= 1.71 \times 10^3$$

$$\therefore r = 1710\ \Omega$$

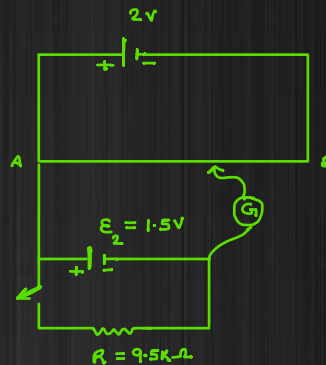

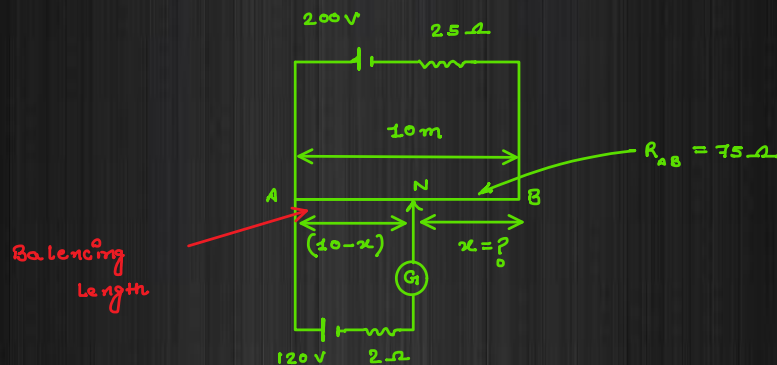Q:  $\rightarrow$  find the value of  $x$ , if  $N$  is the null point.




after finding the null point

$$E = \phi = \frac{l}{AN}$$

$$120 = \phi = (10-x) \quad \text{--- (1)}$$

To find the potential gradient of the P.M wire, considering the primary circuit in open circuit condition

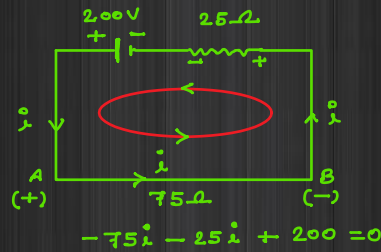considering the primary circuit in open circuit condition of the secondary cell.



$$-75i - 25i + 200 = 0$$

$$\therefore i = \frac{200}{100} = 2 \text{ A} \quad \text{--- (2)} ; \text{ current in the primary circuit}$$

$\therefore$  potential gradient of the wire

$$\phi = \frac{V_{AB}}{L_{AB}} = \frac{i \times R_{AB}}{L_{AB}} = \frac{2 \times 75}{10}$$

$$\therefore \phi = 15 \text{ V/m} \quad \text{--- (3)}$$


from ① & ②

$$120 = 15 \times (10 - x)$$

$$30 = 15x$$

$$\therefore x = \frac{30}{15} = 2 \text{ m}$$

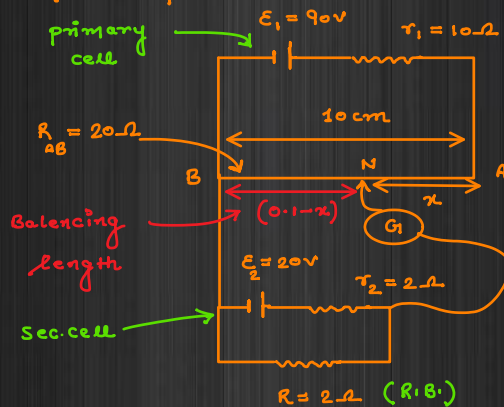Q: find the value of  $x$ , if  $N$  is the Null point.



$\therefore$  internal resistance of the secondary cell

$$r = R \cdot \left\{ \frac{l_c}{l} - 1 \right\} \quad \text{--- (1)}$$


$$\text{here: } \frac{l_c}{l} = (0.1 - x) ; l_c = ?$$

if we balance the sec. cell only;

$$E_2 = \phi \times l_c$$

$$\Rightarrow 20 = \phi \times l_c \quad \text{--- (2)}$$

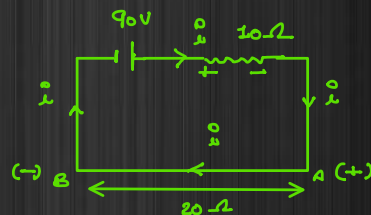for potential gradient of the P.M. considering the primary circuit only in the open circuit condition of the sec. circuit.



$$-10i - 20i + 90 = 0$$

$$i = \frac{90}{30}$$

$$\therefore i = 3 \text{ A} ; \text{ current in the primary circuit}$$

$\therefore i = 3 \text{ A}$  ; current in the primary circuit

so potential gradient of the wire

$$\phi = \frac{V_{AB}}{L_{AB}} = \frac{i \times R_{AB}}{L_{AB}} = \frac{3 \times 20}{0.1} = 600 \text{ V.m}^{-1} \quad \text{--- (3)}$$

from (2) & (3)

$$20 = 600 \times l_c$$

$$\therefore l_c = \frac{20}{600} = \frac{1}{30} \text{ m} ; \text{ balancing length of cell.}$$

from (1)

$$2 = 2 \times \left\{ \frac{1}{30 \times (0.1 - x)} \right\}^{-1}$$


$$1 = \frac{1}{3 - 30x} - 1$$

$$2 = \frac{1}{3 - 30x}$$

$$6 - 60x = 1$$

$$\therefore x = \frac{5}{60} = \frac{1}{12} = 0.083 \text{ m} = 8.33 \text{ cm.}$$

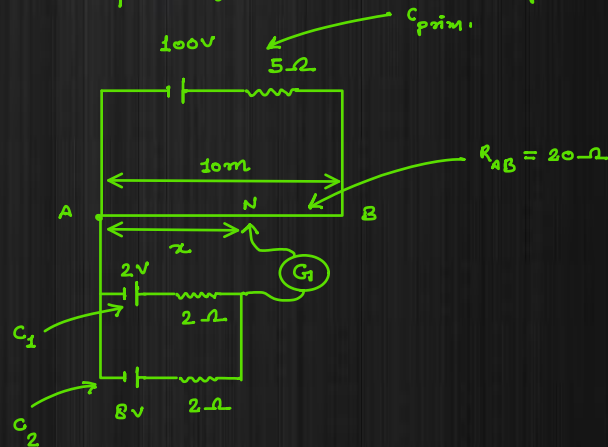Q:  $\rightarrow$  find  $x$  if  $N$  is null point for the combination of cells shown




Sol<sup>n</sup>:  $\rightarrow$  here;  $E_{eq} = \left\{ \frac{E_1}{r_1} + \frac{E_2}{r_2} \right\} = \left( \frac{2}{\frac{1}{2}} + \frac{8}{\frac{1}{2}} \right) = \frac{(1+4)}{1} = 5 \text{ V}$ ; equivalent EMF of the cell combination  
 $C_1$  &  $C_2$  are in parallel  $\left\{ \frac{1}{r_1} + \frac{1}{r_2} \right\}$

as this cell combination get balanced

$$E_{eq} = \phi \times l_{AN}$$

$$5 = \phi \times x \quad \text{--- (1)}$$

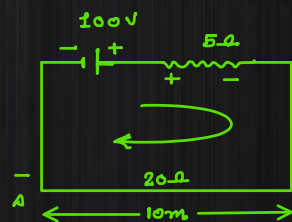for the primary circuit in open circuit condition for the cells  $C_1$  &  $C_2$



$$-5i - 20i + 100 = 0$$

$$\Rightarrow i = \frac{100}{25} = 4 \text{ Amp} \quad \text{--- (2)}$$

so potential gradient of the wire

$$\phi = \frac{V_{AB}}{L_{AB}} = \frac{i \times R_{AB}}{L_{AB}} = \frac{4 \times 20}{10} = 8 \text{ V.m}^{-1} \quad \text{--- (3)}$$

from (1) & (3)

$$5 = 8 \times x$$

$$\therefore x = \frac{5}{8} \text{ m}$$


$$5 = 8 \times x$$

$$\therefore x = \frac{5}{8} \text{ m}$$


Q: A potentiometer wire AB is 100cm long & has a total resistance of  $10\Omega$ . If the null point is found at 40cm, find the value of resistance R.

Soln:  $\rightarrow$

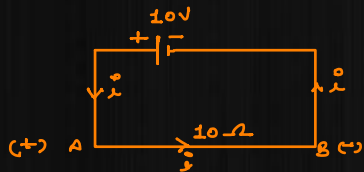potential gradient of the wire in open circuit condition


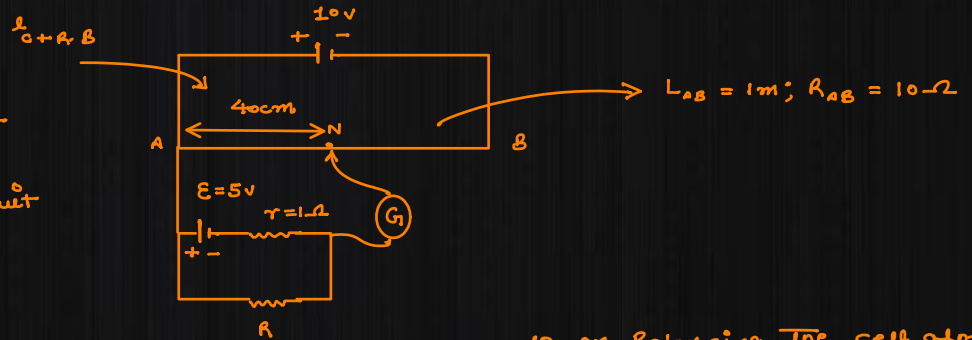
$$\phi = \frac{V_{AB}}{L_{AB}} = \frac{10}{1} = 10 \text{ V} \cdot \text{m}^{-1} \quad \text{--- (1)}$$



so on balancing the cell alone;

$$\varepsilon = \phi \times l_{\text{cell}}$$

$$\text{so } l_{\text{cell}} = \frac{5}{10} = \frac{1}{2} = 0.5 \text{ m} \quad \text{--- (2)}$$

ie; Balancing length of the cell alone.

if we balance the (cell + R) together;

$$r = R \cdot \left\{ \frac{l_c}{l_{c+R}} - 1 \right\}$$

$$\Rightarrow 1 = R \cdot \left\{ \frac{0.5}{0.4} - 1 \right\}$$

$$\Rightarrow 1 = R \times \frac{0.1}{0.4}$$

$$\therefore R = 4 \Omega$$