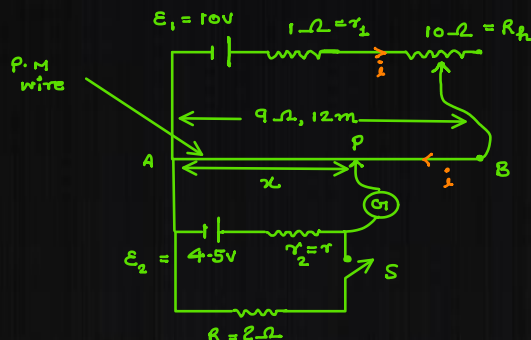


# METER BRIDGE

08 August 2020 11:30

- Q: In the primary circuit of potentiometer the rheostat can be varied from 0 to  $10\Omega$ . Initially it was at 0 resistance.
- find the length AP of the wire such that the  $G_1$  shows zero deflection.
  - Now the Rheostat is put at the maximum resistance i.e.  $10\Omega$  & the switch S is closed. New balancing length is found to be 8m. find the internal resistance  $r$  of the 4.5V cell.



∴ Potential gradient of P.M. wire

$$\phi = i \times \frac{\rho}{A}$$

$$\Rightarrow \phi \propto i$$


on changing the Rheostat  $i$  will change as well as  $\phi$ .

- a) when S is open, we are balancing only the cell.

$$\Rightarrow E = \phi \times l_{\text{cell}}$$

$$\Rightarrow 4.5 = \phi \times x \quad \text{--- (1)}$$

for  $\phi$ ; open the sec. circuit.

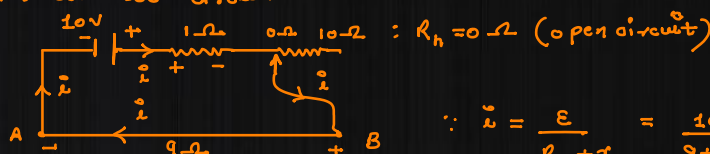

$$\therefore i = \frac{E}{R + r} = \frac{10}{9 + 1} = 1A$$

$$\therefore \phi = \frac{V_{AB}}{L_{AB}} = \frac{i \times R_{AB}}{L_{AB}} = \frac{1 \times 9}{12}$$


$$\text{p.grad of } \phi = \frac{3}{4} \text{ V.m}^{-1} \quad \text{--- (2)}$$

from (1) & (2)

$$4.5 = \frac{3}{4} \times x$$

$x = 6\text{m}$ ; balancing length of the cell alone.

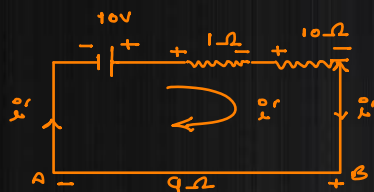- b) for new  $\phi$  (as we change the  $R_h$ , the current in P.M. wire change)



new current in P.M. wire

$$i' = \frac{E}{\{(R_w + R_h) + r\}} = \frac{10}{20} = 0.5A$$

$$\therefore \text{new p.grad. of the wire } (\phi') = \frac{V_{AB}}{L_{AB}} = \frac{i' \times R_{AB}}{L_{AB}} = \frac{0.5 \times 9}{12} \text{ V.m}^{-1} \quad \text{--- (3)}$$


∴ when we balance (cell + R.B) comb.

$$r = R \cdot \left\{ \frac{l_c}{l_c + R.B} - 1 \right\}$$


$$\therefore r = 2 \times \left\{ \frac{12}{8} - 1 \right\} = \frac{2}{8} \times 4 = 1\Omega$$

- Q: In the arrangement shown in the fig. when the switch  $S_2$  is open, balancing length is found  $\frac{L}{2}$ , when the switch  $S_2$  is closed balancing length becomes  $\frac{5L}{12}$ . Find:
- the internal resistance of the cell is 6V.
  - EMF of the primary cell.

Sol: →

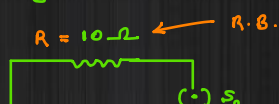

Sol<sup>n</sup>:->

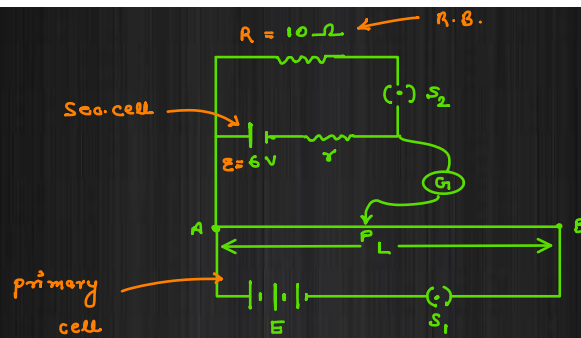

a) Given:  $L_c = \frac{L}{2}$  &  $L_c + R_{AB} = \frac{5L}{12}$

$$\therefore r = R \cdot \left\{ \frac{L_c}{L_c + R_{AB}} - 1 \right\}$$

$$= 10 \cdot \left\{ \frac{\frac{L}{2} \times \frac{12}{5L} - 1 \right\}$$

$$= 10 \cdot \left\{ \frac{6}{5} - 1 \right\}$$

$$= 10 \times \frac{1}{5}$$

Internal resistance ( $r$ ) = 2 ohms

b)



$$\therefore (\Delta V_{AB})_{\text{wire}} = (\Delta V_{AB})_{\text{cell}}$$

$$\therefore V_{AB} = E$$

$\therefore$  potential gradient of the p.m. wire

$$\phi = \frac{V_{AB}}{L_{AB}} = \frac{E}{L} \quad \text{--- (1)}$$


on balancing the secondary cell;

$$E = \phi \times L_{AN}$$

$$6 = \frac{E}{L} \times \frac{L}{2}$$

EMF of the primary cell  $\therefore E = 12$  volt

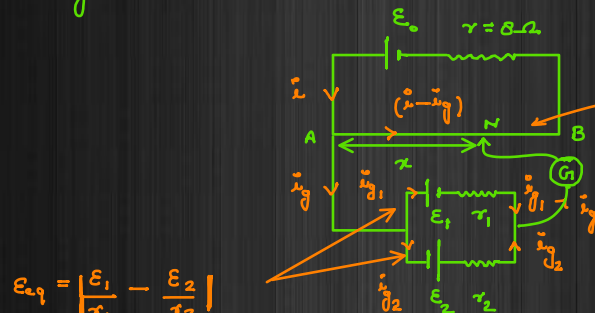Q:-> A battery of EMF  $E_0 = 12V$  is connected across a 4m long wire having resistance  $4 \frac{\Omega}{m}$ . The cells of EMF  $E_1 = 4V$  &  $E_2 = 2V$  having internal resistances  $r_1 = 6 \Omega$  &  $r_2 = 2 \Omega$  respectively are connected as shown in the fig. find the balancing length.



$$E_{eq} = \left| \frac{E_1}{r_1} - \frac{E_2}{r_2} \right|$$

$$\left( \frac{1}{r_1} + \frac{1}{r_2} \right)$$

$$= \left| \frac{4}{6} - \frac{2}{2} \right| = \left| \left( \frac{2}{3} - 1 \right) \right| = \frac{1}{3} \times \frac{3}{2}$$

$$\left( \frac{1}{6} + \frac{1}{2} \right) \frac{4}{6}$$

$$E_{eq} = 0.5 \text{ volt} \quad \text{--- (1)}$$


EMF of sec. cells

$$L_{AB} = 4m; \quad \frac{R_{AB}}{L_{AB}} = \frac{4 \Omega}{m}$$

$$\Rightarrow R_{AB} = 4 \times L_{AB} = 16 \Omega$$

to calculate  $\phi$  opening the sec. circuit;

$$E_0 = 12V \quad r = 8 \Omega$$

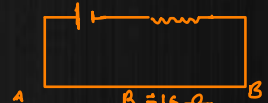

$$\therefore i = \frac{E_0}{R + r} = \frac{12}{24} = 0.5A$$

$$\therefore \phi = \frac{V_{AB}}{L_{AB}} = i \times R_{AB} = 0.5 \times 4 = 2V/m \quad \text{--- (2)}$$

$$\text{pot grad. of the wire} \quad \therefore E_{eq} = \phi \times L_{AN}$$

$$0.5 = 2 \times L_{AN}$$

$$\therefore L_{AN} = \frac{1}{4} = 0.25m$$

Meter Bridge :->

it is a device which is used to determine any unknown resistance.


Known Resistance  $R$  ohms  $\rightarrow$   $R \cdot B$

Unknown Resistance  $X$  ohms  $\rightarrow$   $X \cdot B$

Meter Bridge  $\rightarrow$

It is a device which is used to determine any unknown resistance.

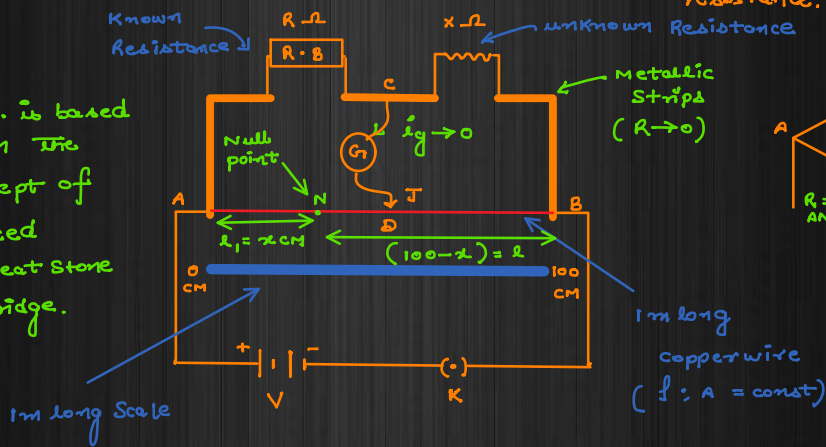Concept  $\rightarrow$  M.B. is based upon the concept of balanced wheat stone Bridge.



if  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$   
 then  $V_C = V_D$  i.e.  $\Delta V_{CD} = 0$   
 then  $i_g = 0$   
 then the w-s bridge is balanced.

$$R_{AN} = \frac{l}{A} \cdot l_{AN} = \frac{l}{A} \cdot x \quad \text{--- (1)} \quad \text{and} \quad R_{NB} = \frac{l}{A} \cdot l_{NB} = \frac{l}{A} \cdot (100-x) \quad \text{--- (2)}$$

as  $G$  shows zero deflection:

$\Rightarrow$  Meter Bridge becomes balanced.

Then:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\Rightarrow \frac{R}{x} = \frac{R_{AN}}{R_{NB}}$$

from (1) & (2)

$$\frac{R}{x} = \frac{x}{(100-x)}$$

$$\therefore \frac{R}{x} = \frac{l_{AN}}{l_{NB}} \quad \text{or} \quad \frac{R_1}{R_2} = \frac{l_1}{l_2}$$

$$x = R \times \frac{(100-x)}{x} \quad \text{--- (3)}$$

here:  $x$  is the position of null point from 0cm mark.

Q:  $\rightarrow$  for a M.B. the known resistance of  $10 \Omega$  & unknown resistance is  $x \Omega$ . when their places in the M.B. get interchanged, the null shifts by  $10 \text{ cm}$ . find:


i) Balancing length in the first case

ii) value of  $x$ .

Given:  $x > 10 \Omega$ .

Sol:  $\rightarrow$

case (1)  $\rightarrow$

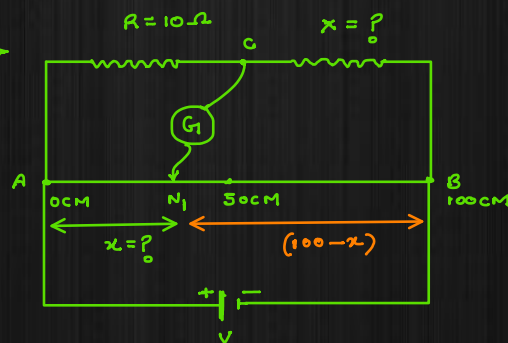



$$\therefore \frac{R}{x} = \frac{l_{AN1}}{l_{N1B}}$$

$$\frac{10}{x} = \frac{x}{(100-x)} \quad \text{--- (1)}$$

case 2:  $\rightarrow$

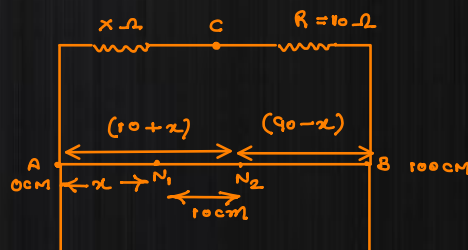when positions of the resistances are interchanged, the position of the new null point further increases by  $10 \text{ cm}$  as  $x > R$



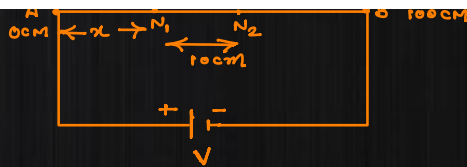

here:  $\frac{x}{R} = \frac{l_{AN_2}}{l_{N_2C}}$

$$\Rightarrow \frac{x}{10} = \frac{(10+x)}{(90-x)} \quad \text{--- ②}$$

from ①  $\times$  ②

$$1 = \frac{x}{(100-x)} \times \frac{(10+x)}{(90-x)}$$

$$9000 - 190x + x^2 = 10x + x^2$$

$$9000 = 200x$$

$$\therefore x = 45 \text{ cm.} \quad \text{--- ③}$$

position of the null point in the initial case

from eqn ①

$$\frac{10}{x} = \frac{45}{(100-45)}$$

$$\Rightarrow x = \frac{10 \times 55}{45}$$

$$= \frac{110}{9}$$

unknown Resistance  $\Rightarrow x = 12.2 \Omega$