

cell \rightarrow it is a device which supplies electric current in the circuit.
It converts chemical energy into electric energy.
Components of any cell are as following \rightarrow

Electro-motive force (EMF) \mathcal{E} \rightarrow It is the potential difference b/w the terminals of a cell in its open circuit condition i.e., when not connected in the circuit.

or
The potential difference b/w its terminals in ideal conditions
its unit is volt.

Internal Resistance (r) \rightarrow it is the resistance offered by the electrolytes of any cell. Its unit is Ohm.



$$\overleftarrow{\Delta V_{\text{open}}} = \mathcal{E} \rightarrow$$

Cell in a circuit i) Discharging cell \rightarrow it is the state in which cell converts chemical energy into electric energy i.e. current flows out of it.




P.D. b/w the terminals of the cell \rightarrow

$$(\Delta V_{AB}) = (\mathcal{E} - i \cdot r) \text{ volt}$$

Discharging \rightarrow (*)

In this condition the current flows from cathode to Anode outside the cell & from anode to cathode inside the cell.

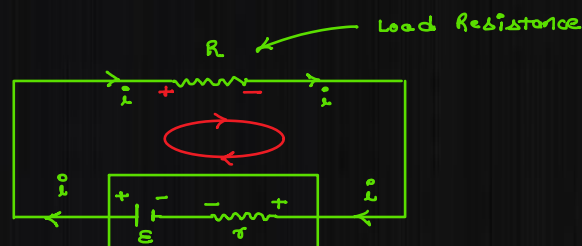current from a discharging cell \rightarrow



from KVL \rightarrow

$$-iR - i \cdot r + \mathcal{E} = 0$$

$$\Rightarrow i(r + R) = \mathcal{E}$$

current discharged by cell $\therefore i = \frac{\mathcal{E}}{(R+r)}$ — (1)

Imp. concept \rightarrow

Power developed across the load resistor

$$P = i^2 \cdot R$$

$$\Rightarrow P = \frac{\mathcal{E}^2}{(R+r)^2} \cdot R \text{ — (1)}$$

for Maximum Power across the load

$$\frac{dP}{dR} = 0$$

for Maximum Power across The load

$$\frac{dP}{dR} = 0$$

$$\Rightarrow \epsilon^2 \cdot \left[\frac{(R+r)^2 - 2(R+r) \cdot R}{(R+r)^4} \right] = 0$$

$$\Rightarrow (R+r)^2 - 2R \cdot (R+r) = 0$$

$$\Rightarrow (R+r)^2 = 2R \cdot (R+r)$$

$$\Rightarrow R+r = 2R$$

$$\Rightarrow r = R \quad \text{--- ②}$$


from ① & ②

$$\therefore P_{\max} = \frac{\epsilon^2 \cdot R}{(R+R)^2} = \frac{\epsilon^2}{4R} \quad \text{or} \quad \frac{\epsilon^2}{4r} \quad \text{watt} \quad \text{--- ③}$$

so if we keep the load resistance equal to the internal resistance, (ie $r=R$) then the power developed across it will be Maximum & equal to $\frac{\epsilon^2}{4r}$ or $\frac{\epsilon^2}{4R}$.

Short circuit current: \rightarrow

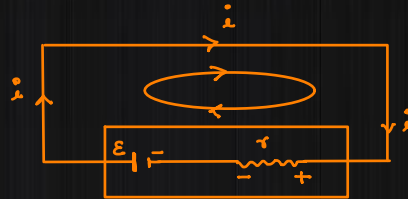if we connect the terminals of a cell's terminals with a connecting wire then the current in the cell is called short-circuit current.



$$-i \cdot r + \epsilon = 0$$

$$\Rightarrow \frac{i}{\text{s.c.}} = \frac{\epsilon}{r} \quad \text{--- ④}$$

ii) charging of a cell: \rightarrow in this state the electric energy into chemical energy ie the current flows inside the cell.

The current flows cathode to anode inside the cell & from anode to cathode outside the cell.




$$\Delta V = (\epsilon + i \cdot r)$$

charging
P.D. b/w the terminals of the cell.

combination of cells: \rightarrow

Combination of cells is called a battery. There are two types of combinations as following.

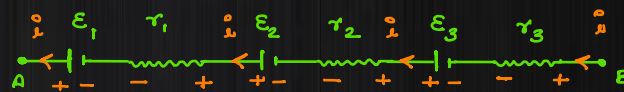
i) series combination: \rightarrow in this combination the current through each cell is same.



P.D. b/w points B & A: \rightarrow

$$\Delta V_{AB} = (-i r_3 + \epsilon_3) + (-i r_2 + \epsilon_2) + (-i r_1 + \epsilon_1)$$
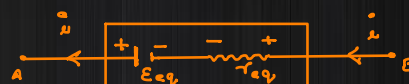
$$\Delta V_{AB} = (\epsilon_1 + \epsilon_2 + \epsilon_3) - i \cdot (r_1 + r_2 + r_3) \quad \text{--- ①}$$



Equivalent cell

for equivalent cell;

$$\Delta V_{AB} = (\mathcal{E}_{eq} - i \cdot r_{eq}) \quad \text{--- ②}$$

comparing eqn ① & ②

$$\mathcal{E}_{eq} = (\mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3) \quad \& \quad r_{eq} = (r_1 + r_2 + r_3)$$

formula for eq. EMF

formula for eq. internal Resistance

* if there are 'n' cells in series connected in same order.

$$\text{Then: } \mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3 + \dots + \mathcal{E}_n$$


$$\& \quad r_{eq} = r_1 + r_2 + r_3 + \dots + r_n$$

* if 'n' identical cells of emf 'E' & internal resistance 'r' each are in same order in series.

$$\mathcal{E}_{eq} = \mathcal{E} + \mathcal{E} + \mathcal{E} + \dots + n \text{ times} = n\mathcal{E}$$

$$r_{eq} = r + r + r + \dots + n \text{ times} = n \times r$$

*)

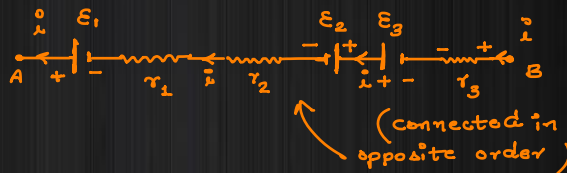

P.D. b/w points B & A \Rightarrow

$$\Delta V_{AB} = (-i r_3 + \mathcal{E}_3) + (-\mathcal{E}_2 - i r_2) + (-i r_1 + \mathcal{E}_1)$$



$$\Rightarrow \Delta V_{AB} = (\mathcal{E}_1 - \mathcal{E}_2 + \mathcal{E}_3) - i(r_1 + r_2 + r_3)$$

$$\text{here: } \mathcal{E}_{eq} = (\mathcal{E}_1 - \mathcal{E}_2 + \mathcal{E}_3) \quad \& \quad r_{eq} = (r_1 + r_2 + r_3)$$

formula for equivalent EMF

formula for equivalent resistance

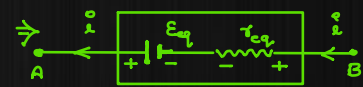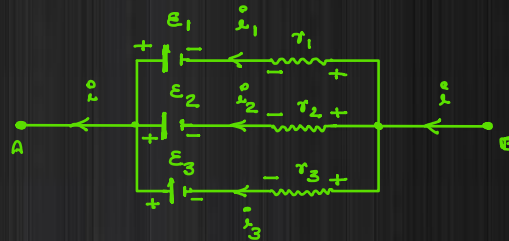ii) Parallel combination \Rightarrow In this type of combination the potential difference across each cell is same.



$$\Delta V_{AB} = (\mathcal{E}_{eq} - i \cdot r_{eq})$$

$$\therefore i = \frac{\mathcal{E}_{eq}}{r_{eq}} - \frac{V}{r_{eq}} \quad \text{--- ④}$$

for cell 1

$$V = \mathcal{E}_1 - i_1 \cdot r_1$$

$$\Rightarrow i_1 r_1 = \mathcal{E}_1 - V$$

$$\therefore i_1 = \frac{\mathcal{E}_1}{r_1} - \frac{V}{r_1} \quad \text{--- ①}$$

for cell 2

$$V = \mathcal{E}_2 - i_2 \cdot r_2$$

$$\therefore i_2 = \frac{\mathcal{E}_2}{r_2} - \frac{V}{r_2} \quad \text{--- ②}$$

for cell 3

$$V = \mathcal{E}_3 - i_3 \cdot r_3$$

$$\therefore i_3 = \frac{\mathcal{E}_3}{r_3} - \frac{V}{r_3} \quad \text{--- ③}$$

from KCL

$$\therefore i = i_1 + i_2 + i_3$$

$$\text{from ①, ②, ③} \& \text{ ④} \Rightarrow \frac{\mathcal{E}_{eq}}{r_{eq}} - \frac{V}{r_{eq}} = \left(\frac{\mathcal{E}_1}{r_1} - \frac{V}{r_1} \right) + \left(\frac{\mathcal{E}_2}{r_2} - \frac{V}{r_2} \right) + \left(\frac{\mathcal{E}_3}{r_3} - \frac{V}{r_3} \right)$$

$$\Rightarrow \left(\frac{\mathcal{E}_{eq}}{r_{eq}} - \frac{V}{r_{eq}} \right) = \left(\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} \right) - V \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)$$

comparing both sides \Rightarrow

$$\text{formula for equivalent resistance} \Rightarrow \frac{1}{r_{eq}} = \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right) \quad \text{--- ⑤}$$

$$\frac{\mathcal{E}_{eq}}{V} = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3}$$

for
Equivalent
resistance

$$\frac{\mathcal{E}_{eq}}{r_{eq}} = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3}$$

$$\therefore \mathcal{E}_{eq} = \frac{\left(\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} \right)}{\frac{1}{r_{eq}}}$$

formula for
Equivalent
EMF

$$\Rightarrow \mathcal{E}_{eq} = \frac{\left(\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} \right)}{\left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)} \quad \text{volt}$$

*) for 'n' cells in parallel:

$$\mathcal{E}_{eq} = \frac{\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} + \dots + \frac{\mathcal{E}_n}{r_n}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots + \frac{1}{r_n}}$$

$$\therefore \frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots + \frac{1}{r_n}$$

*) for 'n' identical cells in parallel each of emf \mathcal{E} & internal resistance 'r' connected in same order.

$$\mathcal{E}_{eq} = \frac{\frac{\mathcal{E}}{r} + \frac{\mathcal{E}}{r} + \frac{\mathcal{E}}{r} + \dots + n \text{ times}}{\frac{1}{r} + \frac{1}{r} + \frac{1}{r} + \dots + n \text{ times}}$$

$$\therefore \mathcal{E}_{eq} = \frac{n \cdot \frac{\mathcal{E}}{r}}{\frac{n}{r}}$$

$$\Rightarrow \mathcal{E}_{eq} = \mathcal{E} \quad \text{---} \textcircled{*}$$

$$\therefore \frac{1}{r_{eq}} = \frac{1}{r} + \frac{1}{r} + \frac{1}{r} + \dots n \text{ times}$$

$$\Rightarrow \frac{1}{r_{eq}} = \frac{n}{r}$$


$$\Rightarrow r_{eq} = \frac{r}{n} \quad \text{---} \textcircled{*}$$

note: if 'n' identical cells of same EMF & internal resistance are connected in same order in parallel combination

then Equivalent EMF will be equal to the EMF of a single cell &

internal Resistance $\frac{1}{n}$ times that of a single cell

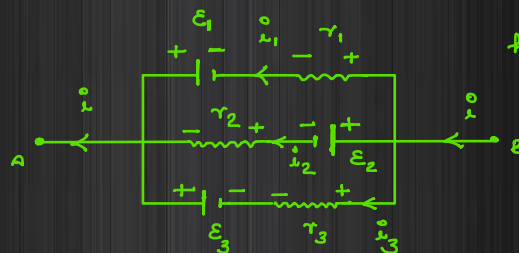*) if any of the cell is connected in opposite order.



$$\text{here; } V = \mathcal{E}_1 - i_1 r_1 \Rightarrow i_1 = \frac{\mathcal{E}_1 - V}{r_1}$$

$$V = -\mathcal{E}_2 - i_2 r_2 \Rightarrow i_2 = -\frac{\mathcal{E}_2 - V}{r_2}$$

$$V = \mathcal{E}_3 - i_3 r_3 \Rightarrow i_3 = \frac{\mathcal{E}_3 - V}{r_3}$$

$$\therefore i = i_1 + i_2 + i_3$$

$$\Rightarrow \left(\frac{\mathcal{E}}{r_{eq}} - \frac{V}{r_{eq}} \right) = \left(\frac{\mathcal{E}_1}{r_1} - \frac{V}{r_1} \right) + \left(-\frac{\mathcal{E}_2}{r_2} - \frac{V}{r_2} \right) + \left(\frac{\mathcal{E}_3}{r_3} - \frac{V}{r_3} \right)$$

$$\Rightarrow \left(\frac{\mathcal{E}_{eq}}{r_{eq}} - \frac{V}{r_{eq}} \right) = \left(\frac{\mathcal{E}_1}{r_1} - \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} \right) - V \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)$$

formula for equivalent EMF

$$\mathcal{E}_{eq} = \frac{\left(\frac{\mathcal{E}_1}{r_1} - \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} \right)}{\left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)}$$

Equivalent internal resistance

$$\frac{1}{r_{eq}} = \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)$$

Q. 'n' numbers of cells are connected in an arrangement as shown in the


$$\left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)$$

$$r_{eq} = \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)^{-1}$$

Q:→ 'N' number of cells are connected in an arrangement as shown in the figure, Emf. of each cell is $\mathcal{E} = \alpha \cdot r$, where α is a constant & r is the internal resistance. Find;

i) the current in the circuit

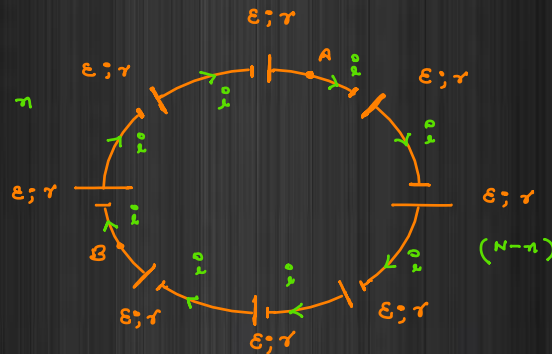ii) if the circuit is divided into n & $(N-n)$ no. of cells b/w points A & B. find the P.D. b/w points A & B.



Solⁿ:→ ∴ all the cells are short-circuited, so let i is the short-circuit current

from KVL

$$\Rightarrow V_1 + V_2 + V_3 + \dots + V_N = 0$$

$$\Rightarrow (\mathcal{E} - ir)_1 + (\mathcal{E} - ir)_2 + (\mathcal{E} - ir)_3 + \dots + (\mathcal{E} - ir)_N = 0$$

$$\Rightarrow N\mathcal{E} - N \cdot i \cdot r = 0$$

$$\Rightarrow i = \frac{N \cdot \mathcal{E}}{N \cdot r} = \frac{\mathcal{E}}{r} = \frac{\alpha \cdot r}{r}$$

$$\therefore i = \alpha \text{ Amp.}$$

ii)

P.D. b/w A & B

$$\Delta V_{AB} = (\mathcal{E} - ir)_1 + (\mathcal{E} - ir)_2 + (\mathcal{E} - ir)_3 + \dots + (\mathcal{E} - ir)_N$$


$$= n \cdot \mathcal{E} - n \cdot i \cdot r$$

$$= n \cdot (\alpha r - \alpha r)$$

$$\Delta V_{AB} = 0 \quad (\text{independent of } n \text{ & } N, \text{ i.e.: P.D. any two points of the given circuit is } 0)$$

Q:→ find the P.D. b/w points A & B.

Solⁿ:→

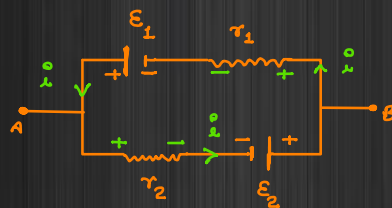

Method 1:→

applying KVL

$$-i r_2 + \mathcal{E}_2 - i r_1 + \mathcal{E}_1 = 0$$

$$\text{Short-circuit current} \Rightarrow i = \left(\frac{\mathcal{E}_1 + \mathcal{E}_2}{r_1 + r_2} \right) \quad \text{--- (1)}$$

$$\Rightarrow \Delta V_{AB} = \mathcal{E}_1 - i r_1 = \mathcal{E}_2 - i r_2$$

$$= \mathcal{E}_1 - \left(\frac{\mathcal{E}_1 + \mathcal{E}_2}{r_1 + r_2} \right) \cdot r_1$$

$$= \frac{(\mathcal{E}_1 r_1 + \mathcal{E}_1 r_2 - \mathcal{E}_1 r_1 - \mathcal{E}_2 r_1)}{(r_1 + r_2)}$$

$$\Rightarrow \Delta V_{AB} = \frac{(\varepsilon_1 r_2 - \varepsilon_2 r_1)}{(r_1 + r_2)} \text{ volts}$$

Method 2: → Equivalent cell: →



$$\text{here; } \varepsilon_{eq} = \left(\frac{\varepsilon_1}{r_1} - \frac{\varepsilon_2}{r_2} \right) \div \left(\frac{1}{r_1} + \frac{1}{r_2} \right) \quad \& \quad r_{eq} = \frac{r_1 r_2}{(r_1 + r_2)}$$


∴ the equivalent cell is open circuit

$$\therefore \Delta V_{AB} = \varepsilon_{eq} - i \cdot r_{eq} \quad ; \text{ here } i = 0$$

$$= \varepsilon_{eq} - 0$$

$$\Delta V_{AB} = \frac{(\varepsilon_1 r_2 - \varepsilon_2 r_1)}{(r_1 + r_2)}$$

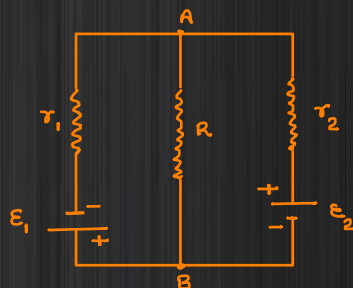Q: find the value of 'R', so that maximum thermal power dissipated in it becomes maximum. find the max. power.



$$\text{Sol}^n \rightarrow \text{for max. power on the load; } R = (r_{\text{cell}})_{eq} = \frac{r_1 r_2}{(r_1 + r_2)} \quad \text{--- (1)}$$

$$\text{also; } P_{\text{Max}} = \frac{\varepsilon_{eq}^2}{4 r_{eq}} \text{ or } \frac{\varepsilon_{eq}^2}{4 R} \quad \text{--- (2)}$$


$$\text{here; } \varepsilon_{eq} = \left(\frac{\varepsilon_1}{r_1} - \frac{\varepsilon_2}{r_2} \right) \div \left(\frac{1}{r_1} + \frac{1}{r_2} \right) = \frac{(\varepsilon_1 r_2 - \varepsilon_2 r_1)}{(r_1 + r_2)} \quad \text{--- (3)}$$

from (2) & (3)

$$\Rightarrow P_{\text{Max}} = \frac{(\varepsilon_1 r_2 - \varepsilon_2 r_1)^2}{(r_1 + r_2)^2 \times 4 r_1 r_2} = \frac{(\varepsilon_1 r_2 - \varepsilon_2 r_1)^2}{4 r_1 r_2 (r_1 + r_2)} \text{ watt}$$

Q: find the current through r_1 & P.D. b/w A & B.

major

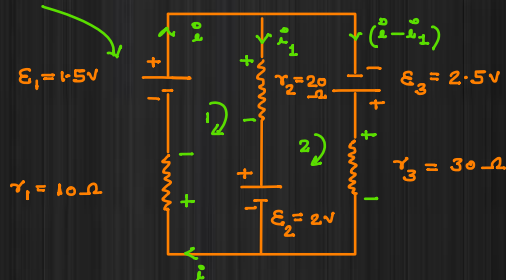

Method ①: (KVL)



from KVL in loop ①

$$-20\vec{i}_1 - 2 - 10\vec{i}_1 + 1.5 = 0$$

$$\Rightarrow 20\vec{i}_1 + 10\vec{i}_1 = -0.5 \quad \text{--- ①}$$

from KVL in loop ②

$$2.5 - (\vec{i} - \vec{i}_1) \times 30 + 2 + 20\vec{i}_1 = 0$$

$$\Rightarrow 50\vec{i}_1 - 30\vec{i} = -4.5 \quad \text{--- ②}$$

$$\text{eqn ①} \times 5 - \text{eqn ②} \times 2$$

$$100\vec{i}_1 + 50\vec{i} = -2.5$$

$$-100\vec{i}_1 - 60\vec{i} = -9$$

$$110\vec{i} = 6.5$$

$$\text{current from } r_1; \therefore \vec{i} = \frac{6.5}{110} \approx 0.06 \text{ A}$$


so P.D. b/w points A & B: \rightarrow

$$\begin{aligned} \Delta V_{AB} &= \varepsilon_1 - \vec{i} \cdot r_1 \\ &= 1.5 - 0.06 \times 10 \\ &= 1.5 - 0.6 \end{aligned}$$

$$\Rightarrow \Delta V_{AB} = 0.9 \text{ volt}$$

Method 2: (cell equivalent) \Rightarrow

considering the equivalent of cell 1 & 2

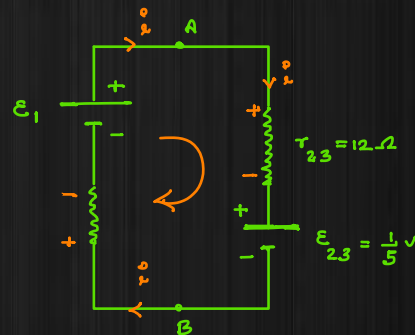

$$\begin{aligned} (\varepsilon_{eq})_{23} &= \left(\frac{\varepsilon_2}{r_2} - \frac{\varepsilon_3}{r_3} \right) = \frac{(\varepsilon_2 r_3 - \varepsilon_3 r_2)}{(r_2 + r_3)} \\ &= \frac{(60 - 50)}{50} = \frac{1}{5} \text{ V} \\ \therefore (r_{eq})_{23} &= \frac{r_2 r_3}{r_2 + r_3} = \frac{600}{50} = 12 \Omega \end{aligned}$$


from KVL


$$-12\vec{i} - 0.2 - 10\vec{i} + 1.5 = 0$$

$$\text{so } \vec{i} = \frac{1.3}{22} = 0.06 \text{ A}$$

$$\therefore \Delta V_{AB} = \varepsilon_1 - \vec{i} \cdot r_1 = 1.5 - 0.06 \times 10 = 0.9 \text{ volt}$$

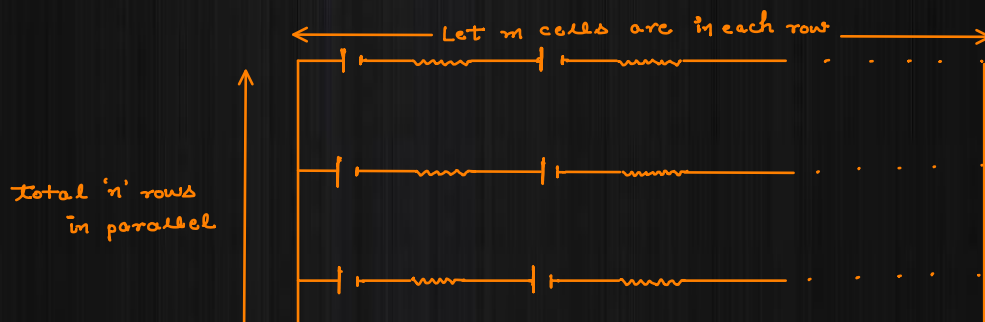Q; find the no. of parallel groups 'n' consisting equal no. of cells in same order joined in series so that maximum power appears on the load of $R = 10 \Omega$, if connected across this battery consisting of 300 identical cells each of internal resistance 'r' where $r = 0.3 \Omega$.



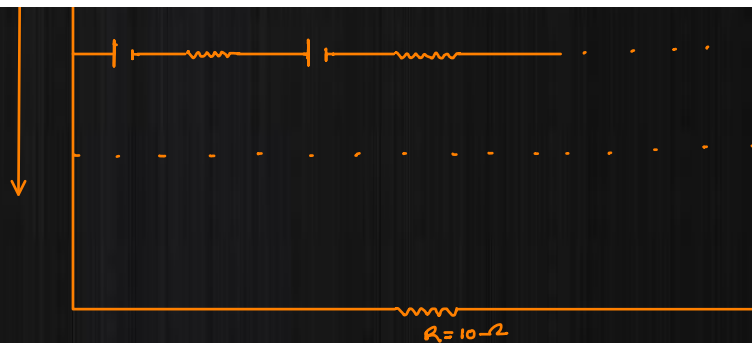

total no. of cells ($m \times n$) = 300

no. of cells in each row ; $m = \frac{300}{n}$ — (1)

equivalent resistance of each row (r_{row}) = $m \times r$

as there are n no. of rows in parallel which are identical

$$\therefore r_{eq} = \frac{r_{row}}{n} = \frac{m \times r}{n} \text{ — (2)}$$

for Max power on the Load;

$$R = r_{eq} = \frac{m \times r}{n}$$


$$10 = \frac{300}{n^2} = 0.3$$

$$\therefore n^2 = 9$$

$$\Rightarrow n = 3$$

Q: find the value of R_x , such that power

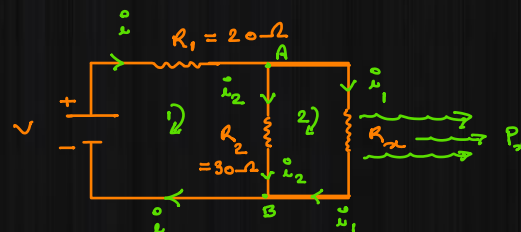developed across it do not depends upon small variation in its value.



R_2 & R_x are in parallel

$$R_{2x} = \frac{R_2 \cdot R_x}{R_2 + R_x}$$

& R_1 & R_{2x} are in series

$$\text{here ; } R_{eq} = R_1 + \frac{R_2 \cdot R_x}{(R_2 + R_x)} = \frac{R_1 R_2 + R_x (R_1 + R_2)}{(R_2 + R_x)} \text{ — (1)}$$

so current withdrawn from the battery

$$i = \frac{V}{R_{eq}} \text{ — (2)}$$

at pt A:

$$\frac{i_1}{i_2} = \frac{R_2}{R_x} \text{ — (3) } \quad \& \quad i_1 + i_2 = i \text{ — (4)}$$

from (3) & (4)

$$i_1 = \frac{R_2 \cdot i}{(R_2 + R_x)} = \frac{R_2}{(R_2 + R_x)} \times \frac{V}{R_{eq}}$$

from (1)

$$\text{current through } R_x \Rightarrow i_1 = \frac{R_2 \cdot V}{R_1 R_2 + (R_1 + R_2) \cdot R_x} \text{ Amp. — (5)}$$

instantaneous power generated on R_x :

$$\Rightarrow P_x = i_1^2 \cdot R_x = \frac{R_2^2 \cdot V^2 \cdot R_x}{\{R_1 R_2 + (R_1 + R_2) \cdot R_x\}^2}$$

as change in R_x do not change P_x

as change in R_x do not change P_x $\{R_1 R_2 + (R_1 + R_2) \cdot R_x\}^{-1}$
 i.e; $\frac{dP_x}{dR_x} = 0$

$$R_2^2 \cdot V^2 \left[\frac{\{R_1 R_2 + (R_1 + R_2) \cdot R_x\}^2 - R_x \times 2 \{R_1 R_2 + (R_1 + R_2) \cdot R_x\} \times (R_1 + R_2)}{\{R_1 R_2 + (R_1 + R_2) \cdot R_x\}^4} \right] = 0$$

$$\Rightarrow \{R_1 R_2 + (R_1 + R_2) \cdot R_x\}^2 - 2 R_x \cdot \{R_1 R_2 + (R_1 + R_2) \cdot R_x\} \cdot (R_1 + R_2) = 0$$

$$\Rightarrow R_1 R_2 + (R_1 + R_2) \cdot R_x = 2 R_x \cdot (R_1 + R_2)$$

$$\therefore R_1 R_2 = R_x \cdot (R_1 + R_2)$$

$$\therefore R_x = \frac{R_1 R_2}{(R_1 + R_2)} = \frac{600}{50} = 12 \Omega$$